

Write a Verilog **STRUCTURAL** model HDL program for an **even up-down Binary counter**. Additional specifications below:

*Implement using D flip flops.

*The sequential circuit has the following inputs: Y, reset, and clock.

*When Y==1 and reset==1, the counter is an upstream state transition:

0000-->0010-->0100-->0110-->1000-->1010-->1100-->1110, back to 0000, and repeat.

*When Y==0 and reset==1, the circuit is a downstream state transition:

1110-->1100-->1010-->1000-->0110-->0100-->0010-->0000, back to 1110, and repeat.

*If reset==0 and regardless of the value of Y, output is 0000.

*reset is a negative edge.

*clock is positive edge with half cycle of 5 time units (i.e., #5 clock = ~clock).

Use the following test cases for the testbench:

- Initially: reset=0, then after 10 time units, change the reset value to 1.
- Then x=0 and ensure enough simulation time to show the entire counter transition.
- Then, x=1 and ensure enough simulation time to show the entire counter transition.
- Print/monitor the value of the inputs (clk, reset, X) and outputs.


Use control transfer construct (i.e., for-loop, repeat, or always) in the testbench. Brute force construct is not allowed.

The Testbench monitor should display all inputs and outputs

Verilog by structural modelling

```
//Consecutive three or more 1's detector using structural modelling
module FF_D(Q,D,clk,rst);
    output reg Q;
    input D, clk, rst;
    always @(posedge clk, negedge rst)
        if (rst==0)
            Q <= 1'b0;
        else
            Q <= D;
endmodule

module detect3(y,A,B,x,clk,reset);
    output y,A,B;
    input x, clk,reset;
    wire DA, DB;
    // assign Flip-flop input and output equations
    assign DA = (A&x) | (B&x);
    assign DB = (A&x) | ((~B)&x);
    assign y = A&B;
    // instantiate D FF
    FF_D F1(A, DA, clk, reset);
    FF_D F2(B, DB, clk, reset);
endmodule
```

 

Testbench

```
//Consecutive three or more 1's detector using structural
modelling (with external input and output w/reset)
module detect3_tb();
    wire t_y;
    wire [1:0] t_state;
    reg t_x, t_clk, t_reset;

    detect3 dut(t_y,t_state[1],t_state[0],t_x,t_clk,t_reset);

    initial
        begin
            t_clk = 1'b0;
            forever #5 t_clk = ~t_clk;
        end

    initial
        begin
            t_reset = 1'b0;
            #20 t_reset = 1'b1;
        end
end
```

```
initial
    begin
        t_x = 1'b1;
        #70 t_x = 1'b0;
    end
initial
    begin
        $display("Program by Sensei RL Uy 3 consecutive 1
detector with external input and output using structural
modelling");
        $monitor("time=%03d, Clk=%b, reset=%b, x=%b,
state=%b, y=%b ", $time, t_clk, t_reset, t_x, t_state, t_y);
        $dumpfile("Seq_io_struct.vcd");
        $dumpvars();
    end

initial #100 $finish;
endmodule
```